



---

**CALIFORNIA STATE UNIVERSITY LONG BEACH**

---

---

**CECS 341 - Computer Architecture and Organization**

**Lab Assignment 3**

**RISC-V**

**Single Cycle Processor**

**(continue)**

Professor: *Maryam S. Hosseini*

Team members:

*Nikki Valerie Benitez*

*Fiona Le*

*Thanh Nguyen*

*Marie Payad*

Due date: 11/27/2020

## I. **Data Memory:**

### 1. **Introduction:**

Data memory stores 128 data each with 32 bits (128 x 32). This block has two tasks, and requires 4 inputs and produces 1 output in total.

- Read data from memory:
  - Inputs:
    - An address that needs to be read (9 bits, addr) - when MemRead is set, this address is the reading address.
    - The read enable signal (MemRead)
  - Output:
    - The data from the address line (read\_data)
- Write data into memory:
  - Inputs:
    - An address that needs to be written (9 bits, addr) - when MemWrite is set, this address is the writing address.
    - The data need to be written into the memory (write\_data)
    - The write enable signal (MemWrite)

### 2. **Procedure:**

- We defined a 128 x 32 2D array called **Memory** to store 128 data each with 32 bits.
- We used @(posedge MemWrite) to check every time that the MemWrite signal is set, then write the data into the memory.
- We also checked that if a MemRead signal is set, read the data from the address line, and write it into the output variable read\_data.

### 3. **Appendix:**

```
`timescale 1ns / 1ps

module DataMem(
    MemRead,
    MemWrite,
    addr,
    write_data,
    read_data
);

    // Define I/O ports
    input      MemRead;    // Control signal for memory read
    input      MemWrite;   // Control signal for memory write
    input [8:0] addr;       // Input Address - 9 LSB bits of the ALU output
    input [31:0] write_data; // Data that needs to be written into the address
```

```

output [31:0] read_data; // Contents of memory location at Address

// Describe data_mem behaviour
// Memory Initialization
reg [31:0] Memory[127:0]; // 128 x 32 memory block

// Memory Write
always @(posedge MemWrite) // write routine, creates flip-flops, Active
high MemWrite
begin
    Memory[addr] <= write_data; // Word written at location addr
end


// Memory Read
assign read_data = (MemRead) ? Memory[addr] : 32'd0;

endmodule

```

## II. Datapath:

### 1. Introduction:

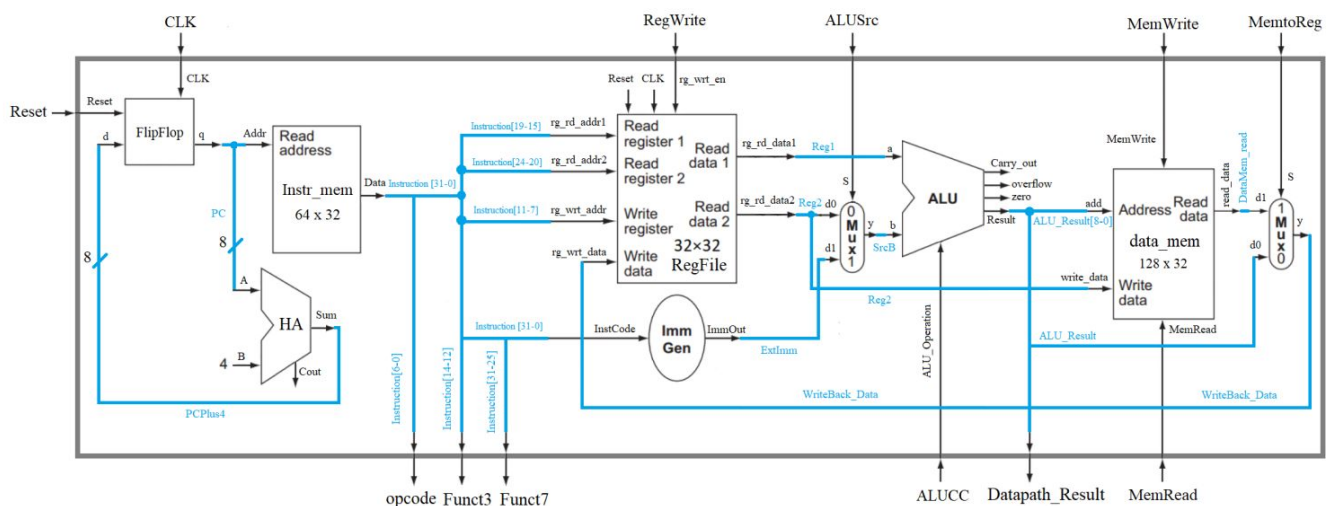

Datapath is the part of the processor that contains the hardware necessary to perform operations required by the processor.

- This module has **8** inputs, some of them (RegWrite, ALUSrc, MemWrite, MemtoReg, MemRead, ALUCC) are control signals which tell the datapath what needs to be done. The other inputs are clock and reset signal.
- It also produces **4** outputs: The Instruction from memory (includes opcode, funct7, and funct3) and the result of ALU (called Datapath\_Result)

### 2. Procedure:

- We used all the submodules (Flip Flop, HA, Instruction Memory, Register File, Immediate Generator, ALU, MUX - two instantiations, Data Memory) as components.
- We used wire to connect all the components to complete the Datapath.
  - First, the instruction execution starts by using the program counter (Flip Flop, HA) to supply the instruction address to the instruction memory.
  - Then based on the Instruction from Instruction Memory, we go over the Register File to get data from memory, and the Immediate Generator to determine which operation needs to execute.
  - If the instruction is an arithmetic-logical instruction, the result from the ALU must be written to a register (ALU\_Result is the output WriteBack\_Data after MUX). If the operation is load or store, the ALU result is used as an address to either store a value from the registers or load a value from memory into the register file (ALU goes into Data Memory as the address line).

### 3. Result:

- Testbench:

```
`timescale 1ns / 1ps

module dp_tb_top();

    /** Clock & reset */
    reg clk, rst;
    always
    begin
        #10;
        clk = ~clk;
    end

    initial
    begin
        clk = 0;
        @(posedge clk);
        rst = 1;
        @(posedge clk);
        rst = 0;
    end

    /** DUT Instantiation */
    wire reg_write;
    wire mem2reg;
    wire alu_src;
    wire mem_write;
```

```
wire      mem_read;
wire [3:0] alu_cc;
wire [6:0] opcode;
wire [6:0] funct7;
wire [2:0] funct3;
wire [31:0] alu_result;

data_path dp_inst(
    .clk(clk),
    .reset(rst),
    .reg_write(reg_write),
    .mem2reg(mem2reg),
    .alu_src(alu_src),
    .mem_write(mem_write),
    .mem_read(mem_read),
    .alu_cc(alu_cc),
    .opcode(opcode),
    .funct7(funct7),
    .funct3(funct3),
    .alu_result(alu_result)
);

/** Stimulus **/
wire [6:0] R_TYPE, LW, SW, RTypeI;

assign R_TYPE = 7'b0110011;
assign LW     = 7'b0000011;
assign SW     = 7'b0100011;
assign RTypeI = 7'b0010011;

assign alu_src  = (opcode == LW || opcode == SW || opcode == RTypeI);
assign mem2reg  = (opcode == LW);
assign reg_write = (opcode == R_TYPE || opcode == LW || opcode == RTypeI);
assign mem_read = (opcode == LW);
assign mem_write = (opcode == SW);

assign alu_cc = ((opcode == R_TYPE || opcode == RTypeI) // add
    && (funct7 == 7'b0000000) && (funct3 == 3'b000)) ? 4'b0010 :
    ((opcode == R_TYPE || opcode == RTypeI) // sub
    && (funct7 == 7'b0100000)) ? 4'b0110 :
    ((opcode == R_TYPE || opcode == RTypeI) // xor
    && (funct7 == 7'b0000000) && (funct3 == 3'b100)) ? 4'b1100 :
    ((opcode == R_TYPE || opcode == RTypeI) // or
    && (funct7 == 7'b0000000) && (funct3 == 3'b110)) ? 4'b0001 :
    ((opcode == R_TYPE || opcode == RTypeI) // and
    && (funct7 == 7'b0000000) && (funct3 == 3'b111)) ? 4'b0000 :
    ((opcode == R_TYPE || opcode == RTypeI) // slt
```


```

    && (funct7 == 7'b0000000) && (funct3 == 3'b010)) ? 4'b0111 :
    ((opcode == R_TYPE || opcode == RTypeI) // nori
    && (funct3 == 3'b100)) ? 4'b1100 :
    ((opcode == R_TYPE || opcode == RTypeI) // ori
    && (funct3 == 3'b110)) ? 4'b0001 :
    ((opcode == R_TYPE || opcode == RTypeI) // addi
    && (funct3 == 3'b010)) ? 4'b0111 :
    ((opcode == LW || opcode == SW) // load or store
    && (funct3 == 3'b010)) ? 4'b0010 : 0;

    initial
    begin
        #420;
        $finish;
    end
endmodule

```

• Waveform:

 

#### 4. Appendix:

```

`timescale 1ns / 1ps

`include "ALU.v"
`include "FlipFlop.v"
`include "Instr_mem.v"
`include "RegFile.v"
`include "Imm_Gen.v"
`include "Mux.v"
`include "Data_mem.v"

module data_path #(
    parameter PC_W      = 8, // Program Counter
    parameter INS_W      = 32, // Instruction Width
    parameter RF_ADDRESS = 5, // Register File Address

```

```
parameter DATA_W      = 32, // Data Write Data
parameter DM_ADDRES    = 9,  // Data Memory Address
parameter ALU_CC_W     = 4   // ALU Control Code Width
) (
    input          clk,      // CLK in Datapath Figure
    input          reset,    // Reset in Datapath Figure
    input          reg_write, // RegWrite in Datapath Figure
    input          mem2reg,   // MemtoReg in Datapath Figure
    input          alu_src,   // ALUSrc in Datapath Figure
    input          mem_write, // MemWrite in Datapath Figure
    input          mem_read,  // MemRead in Datapath Figure
    input [ALU_CC_W - 1:0] alu_cc, // ALUCC in Datapath Figure
    output [6:0] opcode,      // opcode in Datapath Figure
    output [6:0] funct7,     // Funct7 in Datapath Figure
    output [2:0] funct3,     // Funct3 in Datapath Figure
    output [DATA_W - 1:0] alu_result // Datapath_Result in Datapath Figure
);

// Define Datapath Wires
wire [7:0] PC;
wire [7:0] PCPlus4;
wire [31:0] Instruction;
wire [31:0] Reg1;
wire [31:0] Reg2;
wire [31:0] ExtImm;
wire [31:0] WriteBack_Data;
wire [31:0] SrcB;
wire [31:0] ALU_Result;
wire [31:0] DataMem_read;
wire      Carry_out, overflow, zero;

// Assign relationships
// Controller
assign opcode = Instruction[6:0];
assign funct3 = Instruction[14:12];
assign funct7 = Instruction[31:25];

// HA
assign PCPlus4 = PC + 8'd4;

// Flip Flop
FlipFlop flip_flop(
    // inputs
    .clk(clk),      // 1 bit
    .reset(reset),  // 1 bit
    .d(PCPlus4),    // 8 bits
    // output
    .q(PC)          // 8 bits
);
```

```
// Instruction Memory
InstMem instruction_memory(
    // input
    .addr(PC), // 8 bits
    // output
    .instruction(Instruction) // 32 bits
);

// Register File
RegFile register_file(
    // inputs
    .clk(clk), // 1 bit
    .reset(reset), // 1 bit
    .rg_wrt_en(reg_write), // 1 bit
    .rg_wrt_addr(Instruction[11:7]), // 5 bits
    .rg_rd_addr1(Instruction[19:15]), // 5 bits
    .rg_rd_addr2(Instruction[24:20]), // 5 bits
    .rg_wrt_data(WriteBack_Data), // 32 bits
    // outputs
    .rg_rd_data1(Reg1), // 32 bits
    .rg_rd_data2(Reg2) // 32 bits
);

// Mux for ALU
MUX21 mux_src(
    // inputs
    .D1(Reg2), // 32 bits
    .D2(ExtImm), // 32 bits
    .S(alu_src), // 1 bit
    // output
    .Y(SrcB) // 32 bits
);

// Sign Extend
Imm_Gen immediate_generator(
    // input
    .InstCode(Instruction), // 32 bits
    // output
    .ImmOut(ExtImm) // 32 bits
);

// ALU
alu_32 ALU(
    // inputs
    .A_in(Reg1), // 32 bits
    .B_in(SrcB), // 32 bits
    .ALU_Sel(alu_cc), // 4 bits
    // outputs
```



```
.ALU_Out(ALU_Result), // 32 bits
.Carry_Out(Carry_out), // 1 bit
.Zero(zero), // 1 bit
.Overflow(overflow) // 1 bit
);

assign alu_result = ALU_Result;

// Mux for Data memory
MUX21 mux_memory_to_register(
    // inputs
    .D1(ALU_Result), // 32 bits
    .D2(DataMem_read), // 32 bits
    .S(mem2reg), // 1 bit
    // output
    .Y(WriteBack_Data) // 32 bits
);

// Data Memory
DataMem data_memory(
    // inputs
    .MemRead(mem_read), // 1 bit
    .MemWrite(mem_write), // 1 bit
    .addr(ALU_Result[8:0]), // 9 bits
    .write_data(Reg2), // 32 bits
    // output
    .read_data(DataMem_read) // 32 bits
);

endmodule
```